

**EXPERIMENTT NO 9****Design and Implementation of Magnitude Comparator****Objective:-**

To design and implement

2 – Bit magnitude comparator using basic gates.

**Parts required:-**

Sl.No.	COMPONENT	SPECIFICATION	QTY.
1.	AND GATE	IC 7408	2
2.	X-OR GATE	IC 7486	1
3.	OR GATE	IC 7432	1
4.	NOT GATE	IC 7404	1

**Apparatus:-**

- Trainer/ proto board
- Wire cutter
- Patch Cords
- Voltmeter

**THEORY:**

The comparison of two numbers is an operator that determines one number is greater than, less than (or) equal to the other number. A magnitude comparator is combinational circuits that compares two numbers A and B and determine their relative magnitude. The outcome of the comparator is specified by three binary variables that indicate whether

$$A > B, A = B \text{ or } A < B.$$

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

The equality of the two numbers and B is displayed in a combinational circuit designated by the symbol (A=B).

This indicates A greater than B, then inspect the relative magnitude of pairs of significant digits starting from most significant position. A is 0 and that of B is 0.

We have  $A < B$ , the sequential comparison can be expanded as

$$A > B = A_3 B_3^1 + X_3 A_2 B_2^1 + X_3 X_2 A_1 B_1^1 + X_3 X_2 X_1 A_0 B_0^1$$

$$A < B = A_3^1 B_3 + X_3 A_2^1 B_2 + X_3 X_2 A_1^1 B_1 + X_3 X_2 X_1 A_0^1 B_0$$

The same circuit can be used to compare the relative magnitude of two BCD digits.


Where,  $A = B$  is expanded as,




$$A = B = (A_3 + B_3) (A_2 + B_2) (A_1 + B_1) (A_0 + B_0)$$

x<sub>3</sub>      x<sub>2</sub>      x<sub>1</sub>      x<sub>0</sub>

### LOGIC DIAGRAM:

#### 2 BIT MAGNITUDE COMPARATOR

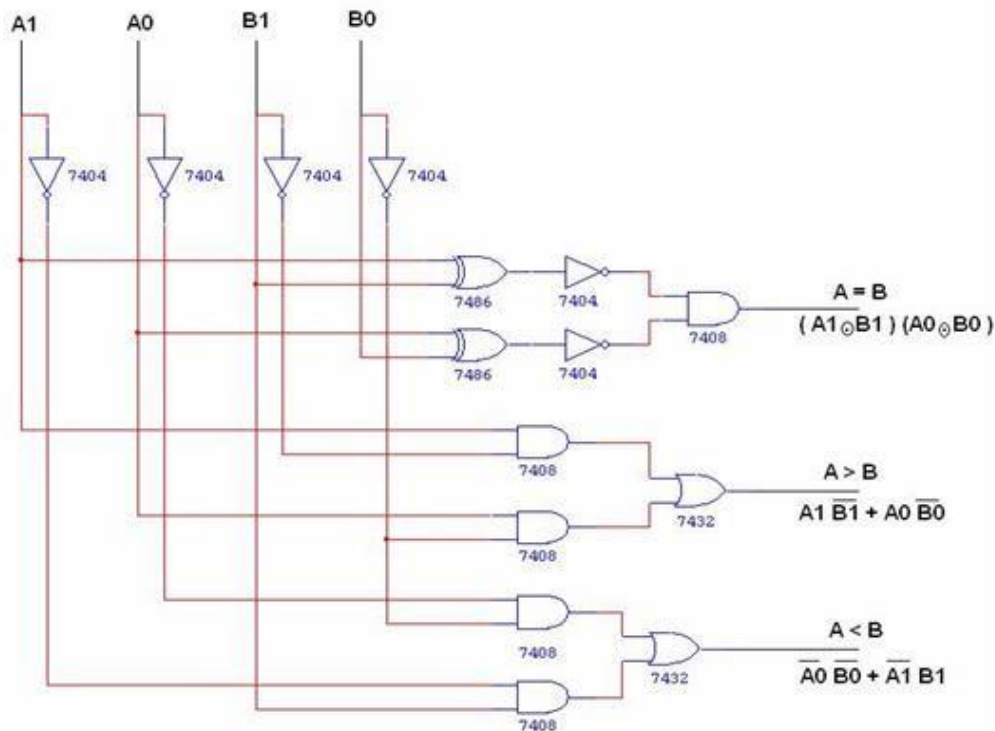

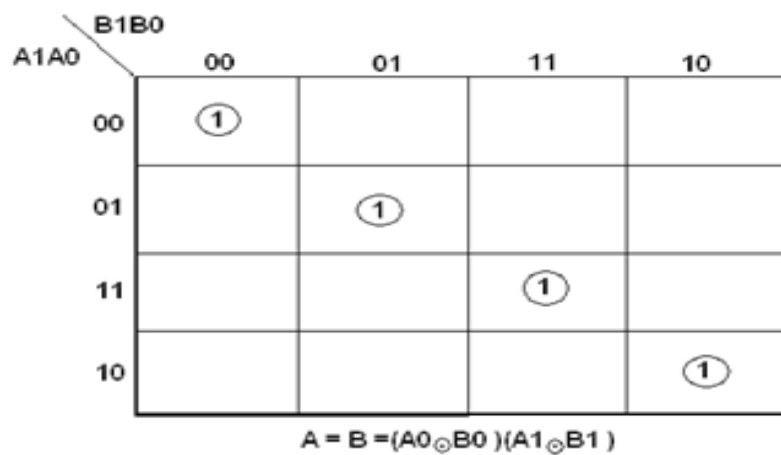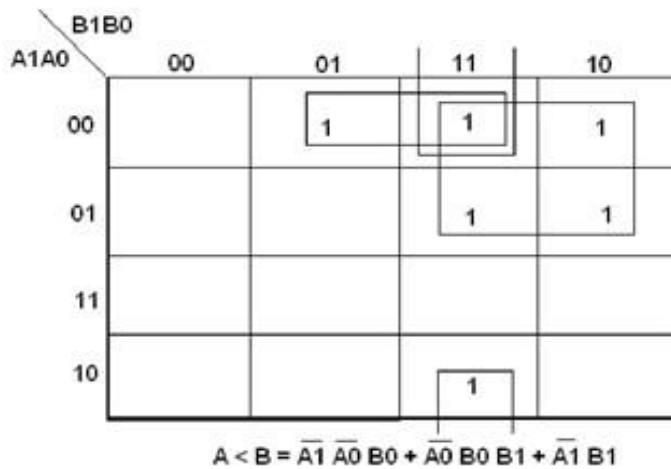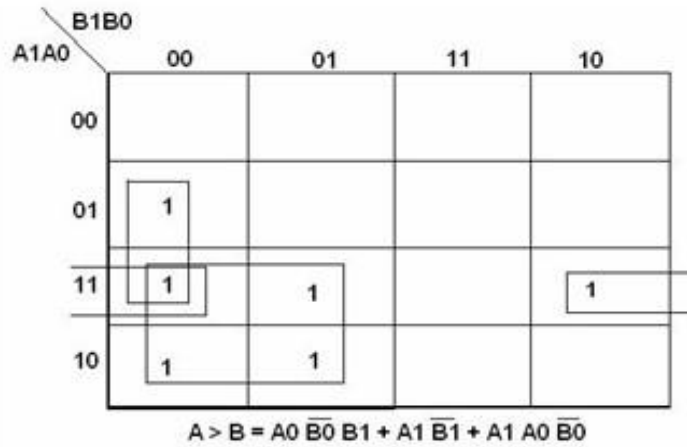**K MAP**

**TRUTH TABLE**

A1	A0	B1	B0	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

**PROCEDURE:**

- (i) Verify the gates
- (ii) Connections are given as per circuit diagram.
- (iii) Logical inputs are given as per circuit diagram.
- (iv) Observe the output and verify the truth table.

**Questions:**