

## EXPERIMENT NO: 5

### Implementation of Adder Half Adder and Full Adder

#### APPARATUS:

7486, 7432, 7408, 7404 IC's, logic kit and connecting leads.

#### HALF ADDER:

Half Adder is combinational logic circuit that generates the sum of two binary numbers (each having 1 bit length). The logic circuit has two inputs and two outputs i.e. Sum & Carry abbreviated as  $S_{HA}$  &  $C_{HA}$  respectively.

First of all, we shall construct Truth Table of Half Adder

Inputs		Output s			
x	y	$S_{HA} = x'y + xy'$		$C_{HA} = x y$	
		Actual	Observed	Actual	Observed
0	0				
0	1				
1	0				
1	1				


Now we write Boolean function from above Truth Table as

$$S_{HA} = x'y + xy'$$

$$C_{HA} = xy$$
 
#### IMPLEMENTATION

Now we implement above Boolean expression by basic logic gates i.e.



Now we shall check this logic circuit by the Truth Table of Half Adder.

**Lab Exercise:**

1. Students are required to write outputs of Full adder using Basic logic gates..
2. Then implement Half Adder using basic logic gates.

**FULL ADDER:**

Full Adder is combination logic circuit that performs the sum of 3 input binary numbers, (each having 1 bit length). Two of the binary input variables are x and y represent the two significant bits to be added the third input z, represents the carry from previous lower significant position. Outputs of Full Adder are Sum and Carry represented as  $S_{FA}$  and  $C_{FA}$  respectively.

First of all, we shall construct Truth Table of Full Adder i.e.

Truth Table						
Input s			Outputs			
x	y	z	$S_{FA}$		$C_{FA}$	
			Actual	Observed	Actual	Observed
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

**Now we write Boolean expression for Sum and Carry of Full Adder.**

$$1) \text{ Sum} = x'y'z + x'yz' + xy'z' + xyz$$

Simplifying by using Boolean Postulates & theorems/k-map, we get

$$\text{Sum} = (x'y + xy')' \cdot z + (x'y + xy') \cdot z'$$

$$S_{FA} = (x \oplus y) \oplus z$$

$$2) \text{ Carry} = x'y'z + x'yz + xy'z' + xyz$$


Simplifying by using Boolean Postulates & theorems/k-map, we get

$$\text{Carry} = (x'y + xy') \cdot z + xy$$

$$C_{FA} = (x \oplus y) z + xy$$
 
### Implementation

Now we implement simplified Boolean expressions of  $S_{FA}$  &  $C_{FA}$  i.e.



We shall check this logic circuit by the Truth Table of Full Adder